

Homework 1


October 25, 2016

Due date: November 8, 2016

- (12%) What are the 8-bit 2's complement representations of the following decimal numbers? Please give both their binary and hexadecimal representations.
 - 95
 - 6
 - 29
- (8%) Prove that (a) $\overline{A}BC + ABC + B\overline{C} = B$ and (b) $A + \overline{A}B = A + B$ using Boolean algebra.
- (8%) A 4-to-2 encoder has four inputs A_3, A_2, A_1, A_0 and two outputs Z_1, Z_0 . Only one of the four inputs can be 1 at a time. Assume that A_i is on, the output (Z_1, Z_0) will correspond to the binary representation of i . For example, when the input $A_2=1$, $(Z_1, Z_0)=(1,0)$ because $10_2 = 2_{10}$. Create the truth table for the 4-to-2 encoder and implement it with logic gates.
- (8%) Design and implement a 4-bit right shifter with sign extension. The inputs are a 2-bit shift amount S_1S_0 and a 4-bit number $X_3X_2X_1X_0$, where X_3 is the MSB. The output is a 4-bit number $Z_3Z_2Z_1Z_0$.
- (10%) In Hack ALU, the following configurations of inputs are used for $x - 1$ and $x - y$. Explain why they work.

zx	nx	zy	ny	f	no	out
0	0	1	1	1	0	$x - 1$
0	1	0	0	1	1	$x - y$

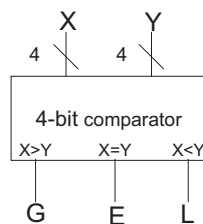- (16%) As shown in the following diagram, design a 4-bit comparator which has two 4-bit unsigned integer inputs, $X_3X_2X_1X_0$ and $Y_3Y_2Y_1Y_0$, and a 3-bit output for the conditions of $X > Y$, $X = Y$ and $X < Y$, respectively. *Hint: design a 1-bit comparator first.*



- (16%) Design a binary multiplier that multiplies two 3-bit unsigned integers, $X = X_2X_1X_0$ and $Y = Y_2Y_1Y_0$, with a 6-bit output $Z = Z_5Z_4 \dots Z_0$ where $Z = X \times Y$; X_0, Y_0 and Z_0 are LSBs. You may use the notation $X[n..m]$ to identify a portion of wires. For example, $X[2..1]$ means the set of wires, X_2X_1 .
- (12%) Refer to the TOY architecture (Figure 1; note that the numbering could be different from the lecture), please specify the operations of MUX_{PC} , MUX_{MEM} , MUX_{REGR} , MUX_{ALU} , MUX_{REGW} , $WRITE_{REG}$, $WRITE_{MEM}$ and ALU_{OP} during the execution stage for the instructions "xor", "store indirect" and "branch if zero". As an example, for "jump and link", they would be $MUX_{PC} = 0$, $MUX_{MEM} = *$, $MUX_{REGR} = *$, $MUX_{ALU} = 1$, $MUX_{REGW} = 01$, $WRITE_{REG} = 1$, $WRITE_{MEM} = 0$, $ALU_{OP} = *$. (For ALU_{OP} , you only need to specify 3-bit $ALU_{control}$ as specified in Figure 1.)

